

What is a series circuit?

What is a parallel circuit?

# Series VS parallel



In what way(s) is a series circuit different from a parallel circuit?

In what way(s) are the circuits similar?

Standards 1STE .1a , 1STE .1.c , 1STE .2.d , 1STE .3a , 1STE .3d , 1STE .4.h

54 Fred